

A decorative graphic on the left side of the slide, consisting of a network of white lines and circles on a dark blue background, resembling a circuit board or a digital signal path.

DIGITAL DESIGN

LAB3 BITWISE OPERATION IN VERILOG, GATES IN RTL VS LUT IN FPGA

2022 FALL TERM

LAB3

- Verilog
 - Bitwise and logic operations in Verilog
- Design mode in Verilog
 - 1. data flow
- Vivado
 - Schematic of “TRL analysis” (Gates)
 - Schematic of “Synthesis” (LUT of FPGA chip)

BITWISE AND LOGICAL OPERATIONS IN VERILOG

Four-valued logic (The IEEE 1364 standard): 0, 1, Z (high impedance), and X (unknown logic value).

Operator : ~ & ^ ~^ ^~ | ! && || 位运算 (比特位运算)

Priority:

~ ! > & > ^ ~^ ^~ > | > && > ||

按位运算

01 & 01 = 01

01 && 01 = 1

Operator type	Operator symbols	Operation performed
Bitwise	~	Bitwise NOT (1's complement)
	&	Bitwise AND
		Bitwise OR
	^	Bitwise XOR
	~^ or ^~	Bitwise XNOR
Logical	!	NOT
	&&	AND
		OR

~ > & > ^ ~^ ^~ > | > && > ||

DESIGN MODE IN VERILOG - DATA FLOW

- 1. Data flow design: using “assign” as *continuous assignment*, to transfer the data from input ports through variables to the output ports .

logical expression	data flow in Verilog
$f(a,b,c) = abc + a'b$	<code>assign f = a & b & c ~a & b;</code>
$f(a,b,c) = \sum(2,4,5,6) = a'bc' + ab'c' + ab'c + abc'$	<code>assign f = ~a & b & ~c a & ~b & ~c a & ~b & c a & b & ~c;</code>


DATA FLOW DESIGN

Demo: a) $q1 = x$ b) $q2 = x + xy$ c) $q3 = x(x + y)$

```
module lab3_df(  
    input x,  
    input y,  
    output q1,  
    output q2,  
    output q3  
);  
    assign q1 = x;  
    assign q2 = x | (x & y);  
    assign q3 = x & (x | y);  
endmodule
```

```
module lab3_df_sim( );  
    reg simx, simy;  
    wire simq1, simq2, simq3;  
    lab3_df u_df(  
        .x(simx), .y(simy), .q1(simq1), .q2(simq2), .q3(simq3) );  
  
    initial  
    begin  
        simx=0;  
        simy=0;  
        #10  
        simx=0;  
        simy=1;  
        #10  
        simx=1;  
        simy=0;  
        #10  
        simx=1;  
        simy=1;  
    end  
endmodule
```

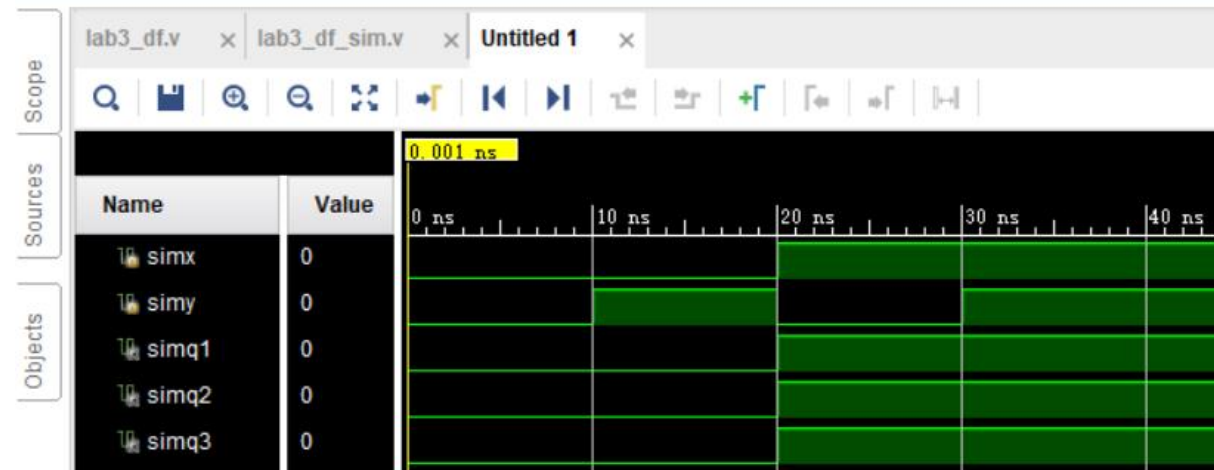SIMULATION - Behavioral Simulation - Functional - sim_1 - lab3_df_sim





SCHEMATIC IN 'RTL ANALYSIS'


LUT: 查找表

RTL: 逻辑门组成的最基内容

```
module lab3_df(  
    input x,  
    input y,  
    output q1,  
    output q2,  
    output q3  
);  
    assign q1 = x;  
    assign q2 = x | (x & y);  
    assign q3 = x & (x | y);  
endmodule
```

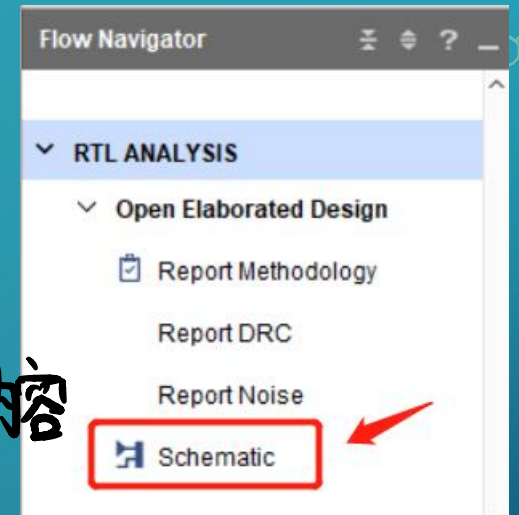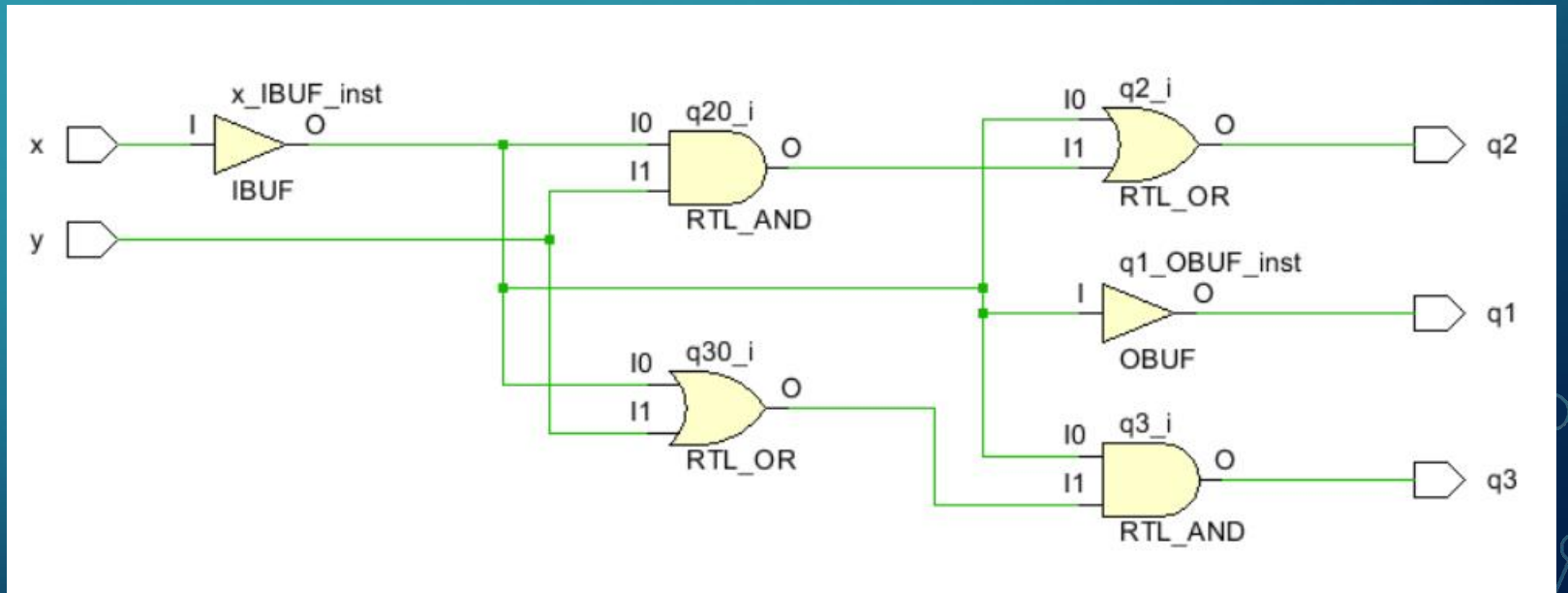

SCHEMATIC IN 'SYNTHESIS'(1)

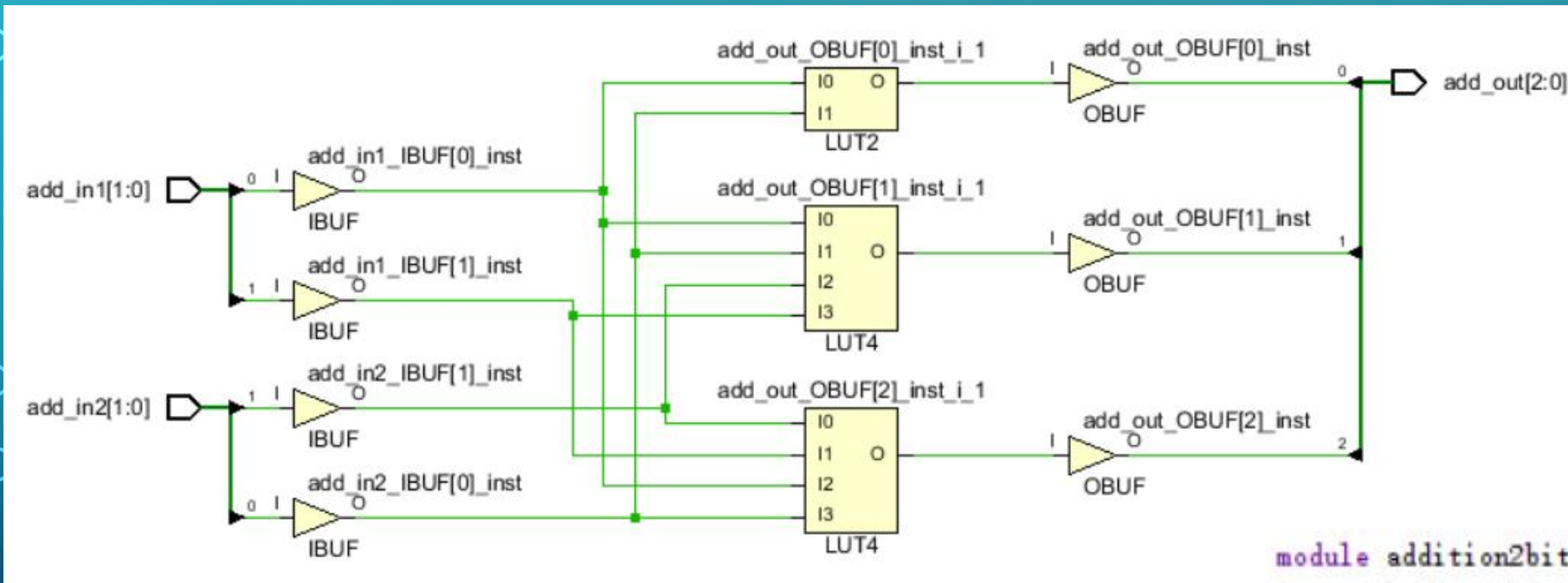


SYNTHESIS

- ▶ Run Synthesis ¹
- ▼ Open Synthesized Design ²
 - Constraints Wizard
 - Edit Timing Constraints
 - Set Up Debug
 - Report Timing Summary
 - Report Clock Networks
 - Report Clock Interaction
 - Report Methodology
 - Report DRC
 - Report Utilization
 - Report Power
 - Schematic ³


```
module addition2bit(  
    input [1:0] add_in1,  
    input [1:0] add_in2,  
    output [2:0] add_out  
);  
    assign add_out = add_in1+add_in2;  
endmodule
```

SCHEMATIC IN 'SYNTHESIS'(2)

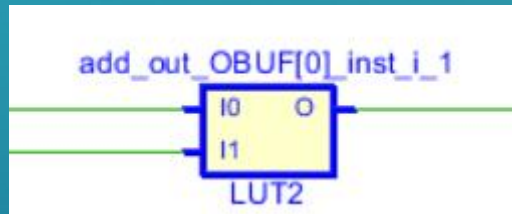- **Double click** the LUT in schematic window



- In the '**Cell Properties**' window , choose '**Truth Table**', the truth table of the cell is shown

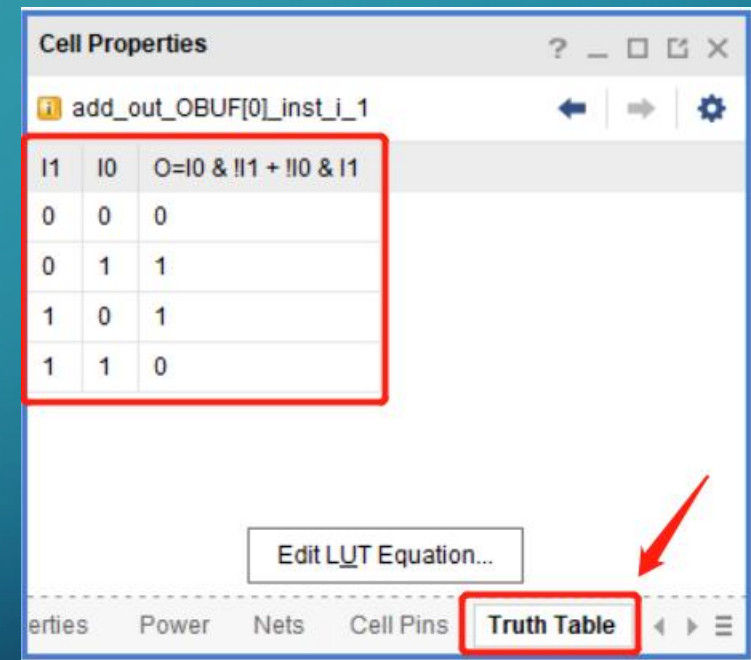

PRACTICE1

- 1. Do the circuit design:
 - There are 3 inputs: x, y and z, 3 output: o1,o2 and o3(all of them are 1 bit width)
 - The logical expression between inputs and outputs are:
$$o1 = xyz + xyz' , o2 = xy(z + z') , o3 = xy$$

Implement the circuit by using data flow

- 2. Get the schematic of the circuit in “RTL analysis” and “Synthesis” respectively, describe the differences between them.

PRACTICE1

- 3. create testbench, do simulation to verify function of the design.
make your conclusion about the following the by using the waveform of simluation.

$$xyz+xyz' = xy(z+z') = xy$$

- 4. generate bitstream file, test the circuit on the board
- 5. For 3 circuit : o1= $xyz+xyz'$, o2= $xy(z+z')$, o3= xy , Which circit is better,why ?

PRACTICE2

- Design a circuit to get the addition of two two-bit unsigned numbers:
 - **In the design, the operator “+” in verilog is not allowed here.**
 - Build a test bench to verify the function of your design.
 - Programme the the FPGA chip with the bitstream file, then test the design.

a[1]	a[0]	b[1]	b[0]	sum[2]	sum[1]	sum[0]
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

TIPS1

- List the Truth-table of the circuit.
- Recode it's logical expression about every bit of output and the inputs.

`sum[0] = ...; sum[1]=....; sum[2]=....;`

`sum[2] = a[1]' a[0] b[1] b[0] +`

`a[1] a[0]' b[1] b[0]' + a[1] a[0] 'b[1] b[0]+`

`a[1] a[0] b[1]' b[0] + a[1] a[0] b[1]' b[0] + a[1] a[0] b[1] b[0]'+a[1] a[0] b[1] b[0];`

- Using bitwise operator “&” ,“|” and “~” to express the logical expression in verilog(Don't forget the keyword “assign” in verilog).


`assign sum[2] = ~a[1] & a[0] & b[1] & b[0] | a[1] & ~a[0] & b[1] & ~b[0] | ...`

a[1]	a[0]	b[1]	b[0]	sum[2]	sum[1]	sum[0]
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

Q: How many gates needed in this circuit ? is it too much ?

PRACTICE3

- Design a circuit to get the addition of two two-bit unsigned numbers:
 - In the design:
 - the operator “+” in verilog is not allowed here.
 - using gates as less as possible.
 - Build a test bench to verify the function of your design.

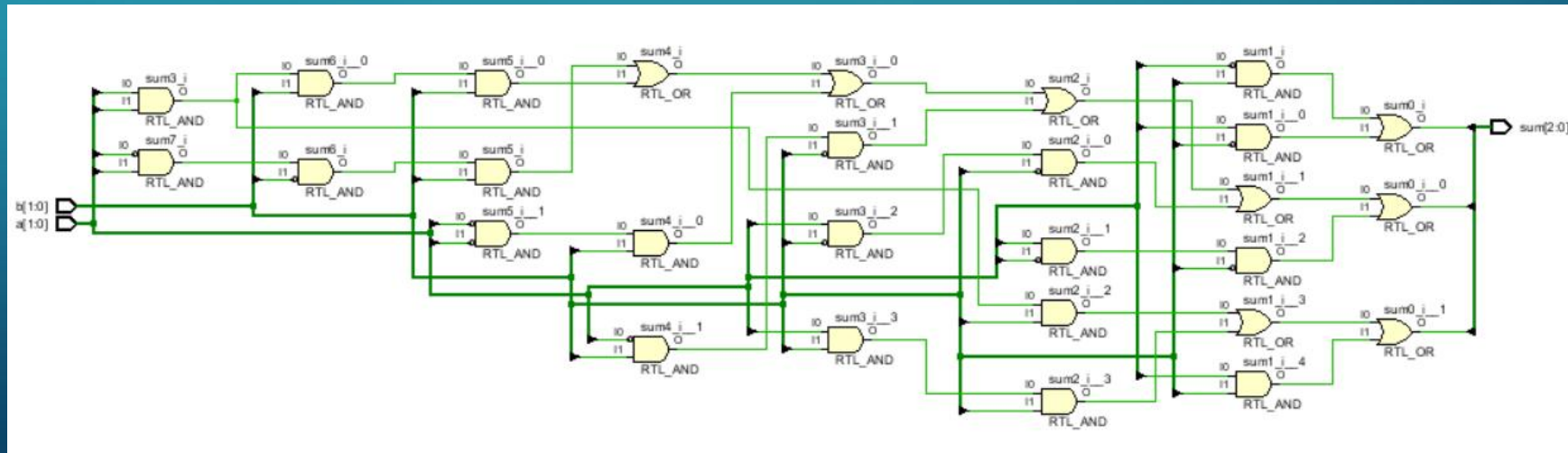

TIP2

- Simplify the circuit by using karnaugh map.

a[1]	a[0]	b[1]	b[0]	sum[0]
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

Before the simplification, there are only ? not gate(s), ? and gate(s) and ? or gate(s) in the circuit.

sum[0]		b[1]b[0]			
		00	01	11	10
a[1]a[0]	00		1	1	
	01	1			1
	11	1			1
	10		1	1	

sum[0]		b[1]b[0]			
		00	01	11	10
a[1]a[0]	00		1	1	
	01	1			1
	11	1			1
	10		1	1	

After simplified by using karnaugh map, the circuit about sum[0] and a,b in Verilog is:

```
assign sum[0]= ~a[0]&b[0] + ~b[0]&a[0];
```

There are only ? not gate(s), ? and gate(s) and ? or gate(s).

证明 De Morgan 定律: 两个输入口, 四个输出口 A . B.

a[1]	a[0]	b[1]	b[0]	sum[1]
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

sum[1]		b[1]b[0]			
		00	01	11	10
a[1]a[0]	00			1	1
	01		1		1
	11	1		1	
	10	1	1		

sum[1]		b[1]b[0]			
		00	01	11	10
a[1]a[0]	00			1	1
	01		1		1
	11	1		1	
	10	1	1		

$$\begin{aligned}
 \text{SUM}[1] = & (\sim a[1] \& a[0] \& \sim b[1] \& b[0]) \mid (a[1] \& a[0] \& b[1] \& b[0]) \mid \\
 & (\sim a[1] \& \sim a[0] \& b[1]) \mid (\sim a[1] \& b[1] \& \sim b[0]) \mid \\
 & (a[1] \& \sim b[1] \& \sim b[0]) \mid (a[1] \& \sim a[0] \& \sim b[1]);
 \end{aligned}$$

a[1]	a[0]	b[1]	b[0]	sum[2]
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

sum[2]		b[1]b[0]			
		00	01	11	10
a[1]a[0]	00				
	01			1	
	11		1	1	1
	10			1	1

sum[2]		b[1]b[0]			
		00	01	11	10
a[1]a[0]	00				
	01			1	
	11		1	1	1
	10			1	1

$$\text{sum}[2] = (a[1]\&a[0]\&b[0]) \mid (a[0]\&b[1]\&b[0]) \mid (a[1]\&b[1])$$