



DIGITAL DESIGN

ASSIGNMENT REPORT

ASSIGNMENT ID : 4

Student Name: 杨钰城

Student ID: 12112323

PART 1: DIGITAL DESIGN THEORY


Provide your answers here:

Assignment 4

- (10 points) Implement a full adder with two 4×1 multiplexers. Draw the logic diagram.

We use one multiplexers to express carry "c" and another expresses output "s"

input variables :			out put	
A	B	X	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

- (10 points) Design a sequence generator to generate the sequence 110101. Draw the logic diagram.

$2^3 - 1 = 6$ we need at least three states but 101 appear twice so we need four states.

a	b	c	d
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

A	B	C	D
1	0	0	1
1	0	0	0
0	1	1	1
0	1	1	0
0	1	0	1
0	1	0	0
0	0	1	1
0	0	1	0
0	0	0	1
0	0	0	0

$$A = \Sigma(0, 1)$$

$$B = \Sigma(2, 3, 4, 5)$$

$$C = \Sigma(2, 3, 6, 7)$$

$$D = \Sigma(0, 2, 4, 6, 8)$$

$$A = a'b'c'$$

$$B = bc' + b'c = b \oplus c$$

$$C = c$$

$$D = d'$$

B:


ab \ cd	00	01	11	10
00	0	0	1	1
01	1	1	0	0
11	x	x	x	x
10	0	0	x	x

C:

ab \ cd	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	x	x	x	x
10	0	0	x	x

D:

ab \ cd	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	x	x	x	x
10	1	0	x	x

 

- (20 points) List the eight unused states in a 4-bit Johnson's counter. Determine the next state for each unused state and show that, if the circuit finds itself in an invalid state, it does not return to a valid state. Then modify the circuit so that the circuit reaches a valid state from any one of the unused states. Draw the logic diagram.

eight unused states

clk	Q _A	Q _B	Q _C	Q _D
X	0	1	0	0
↑	1	0	1	0
↑	1	1	0	1
↑	0	1	1	0
↑	1	0	1	1
↑	0	1	0	1
↑	0	0	1	0
↑	1	0	0	1

all the states are unused states and they will repeat in the unused states and can't change to the valid states.


clk	Q _A	Q _B	Q _C	Q _D	Z	next state
X	0	1	0	0	0	1010
↑	1	0	1	0	0	1101
↑	1	1	0	1	0	0110
↑	0	1	1	0	0	1011
↑	1	0	1	1	0	0101
↑	0	1	0	1	0	0010
↑	0	0	1	0	0	1001
↑	1	0	0	1	0	0100

↑	0	0	0	0	1	$Z = \Sigma(0, 8, 9, 12, 14)$
↑	1	0	0	0	1	
↑	1	1	0	0	1	
↑	1	1	1	0	1	
↑	1	1	1	1	0	
↑	0	1	1	1	0	
↑	0	0	1	1	0	
↑	0	0	0	1	0	



$Q_A Q_B$ \ $Q_C Q_D$	00	01	11	10
00	1	0	0	0
01	0	0	0	0
11	1	0	0	1
10	1	0	0	0

$$Z = Q_B' Q_C' Q_D' + Q_A Q_B Q_D'$$

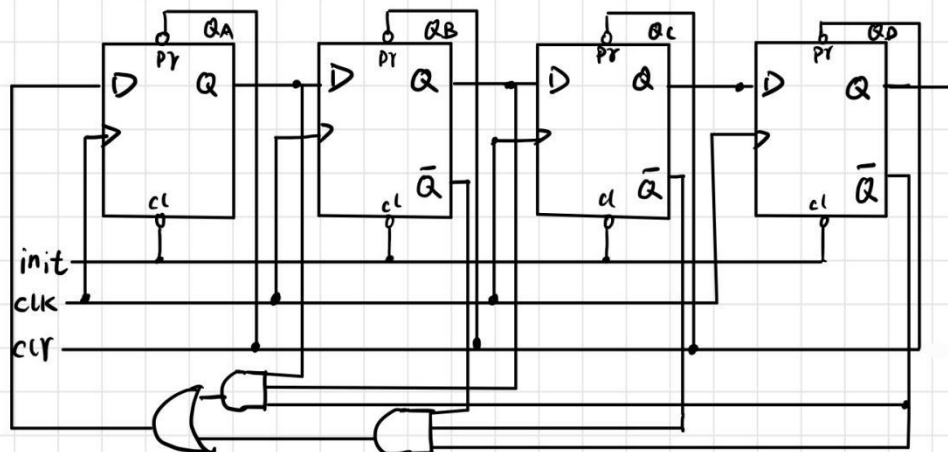

- (20 points) Design a synchronous counter that has the following sequence: 0010, 0110, 1001, 1000, 1100, 1101, and repeat. From the undesired states the counter must always go to 0010 on the next clock pulse. Draw the logic diagram.

	Previous state					next state			
	Q_A	Q_B	Q_C	Q_D		Q_A	Q_B	Q_C	Q_D
0	0	0	0	0		0	0	1	0
1	0	0	0	1		0	0	1	0
2	0	0	1	0		0	1	1	0
3	0	0	1	1		0	0	1	0
4	0	1	0	0		0	0	1	0
5	0	1	0	1		0	0	1	0

6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

1	0	0	1
0	0	1	0
1	1	0	0
1	0	0	0
0	0	1	0
0	0	1	0
1	1	0	1
0	0	1	0
0	0	1	0
0	0	1	0

$$\bar{Q}_A = \sum (6, 8, 12)$$

$$\bar{Q}_B = \sum (2, 3, 12)$$

$$\bar{Q}_C = \sum (0, 1, 2, 3, 4, 5, 7, 8, 10, 11, 13, 14, 15)$$

$$\bar{Q}_D = \sum (6, 12)$$

$Q_C Q_D$	\bar{Q}_A				
$Q_A Q_B$	00	01	11	10	
00	0	0	0	0	
01	0	0	0	1	
11	1	0	0	0	
10	1	1	0	0	

$$Q_A = Q_A Q_C' Q_D' + Q_A Q_B' Q_C' + Q_A' Q_B Q_C Q_D'$$

$Q_C Q_D$	\bar{Q}_B				
$Q_A Q_B$	00	01	11	10	
00	0	0	0	1	
01	0	0	0	0	
11	1	0	0	0	
10	1	0	0	0	

$$Q_B = Q_A Q_C' Q_D' + Q_A' Q_B' Q_C Q_D'$$

$Q_C Q_D$	\bar{Q}_C				
$Q_A Q_B$	00	01	11	10	
00	1	1	1	1	
01	1	1	1	0	
11	0	1	1	1	
10	0	0	1	1	

$$Q_C = Q_B Q_D + Q_A' Q_B + Q_A' Q_C' + Q_A Q_C$$

$Q_C Q_D$	\bar{Q}_D				
$Q_A Q_B$	00	01	11	10	
00	0	0	0	0	
01	0	0	0	1	
11	1	0	0	0	
10	0	0	0	0	

$$\bar{Q}_D = Q_A' Q_B Q_C Q_D' + Q_A Q_B Q_C' Q_D'$$




$$Q_A = Q_A Q_C' Q_D' + Q_A Q_B' Q_C' + Q_A' Q_B Q_C Q_D'$$

$$Q_B = Q_A Q_C' Q_D' + Q_A' Q_B' Q_C Q_D' = (Q_A Q_C' + Q_A' Q_B' Q_C) Q_D'$$

$$Q_C = Q_B Q_D + Q_A' Q_B + Q_A Q_C' + Q_A Q_C$$
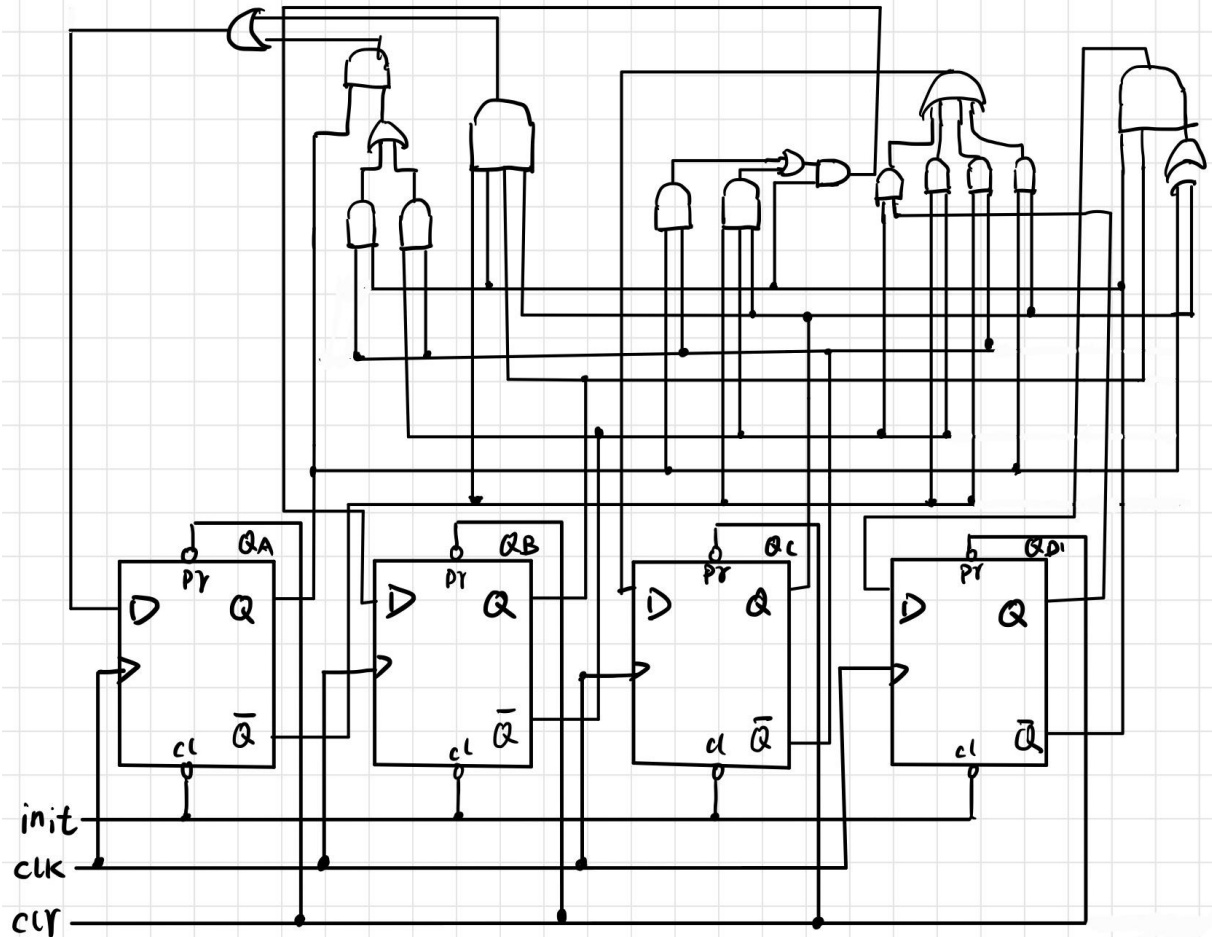
$$Q_D = Q_A' Q_B Q_C Q_D' + Q_A Q_B Q_C' Q_D' = (Q_A \oplus Q_C) Q_B Q_D'$$




- (15 points) Implement a BCD ripple counter using a four bit binary ripple counter with asynchronous clear and external NAND gates. Draw the logic diagram.

$$2^{4-1} < 9 < 2^4$$

use four TFF

 when $Q_3 Q_2 Q_1 Q_0 = 1010$ the counter should be reset



- (15 points) Determine the input equations for a BCD counter that uses

- only JK flip-flops, and
- only D flip-flops.

Compare these two designs and the one given in the lecture that uses only T flip-flops. Determine which one is the most efficient and why.

JK F-F:

present				next				FF input							
A_3	A_2	A_1	A_0	A_3	A_2	A_1	A_0	J_{A_3}	K_{A_3}	J_{A_2}	K_{A_2}	J_{A_1}	K_{A_1}	J_{A_0}	K_{A_0}
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	0	0	1	0	0	0	0	X	1	0	X	0	X	X	1



$A_3A_2 \backslash A_1A_0$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	x	x	x	x
10	x	x	x	x

J_{A_3}

$A_3A_2 \backslash A_1A_0$	00	01	11	10
00	x	x	x	x
01	x	x	x	x
11	x	x	x	x
10	0	1	x	x

K_{A_3}

$A_3A_2 \backslash A_1A_0$	00	01	11	10
00	0	0	1	0
01	x	x	x	x
11	x	x	x	x
10	0	0	x	x

J_{A_2}

$A_3A_2 \backslash A_1A_0$	00	01	11	10
00	x	x	x	x
01	0	0	1	0
11	x	x	x	x
10	x	x	x	x

K_{A_2}

$A_3A_2 \backslash A_1A_0$	00	01	11	10
00	0	1	x	x
01	0	1	x	x
11	x	x	x	x
10	0	0	x	x

J_{A_1}

$A_3A_2 \backslash A_1A_0$	00	01	11	10
00	x	x	1	0
01	x	x	1	0
11	x	x	x	x
10	x	x	x	x

K_{A_1}

$A_3A_2 \backslash A_1A_0$	00	01	11	10
00	1	x	x	1
01	1	x	x	1
11	x	x	x	x
10	1	x	x	x

J_{A_0}

$A_3A_2 \backslash A_1A_0$	00	01	11	10
00	x	1	1	x
01	x	1	1	x
11	x	x	x	x
10	x	1	x	x

K_{A_0}

$$J_{A_3} = A_2A_1A_0$$

$$K_{A_3} = A_0$$

$$J_{A_2} = A_1A_0$$

$$K_{A_2} = A_1A_0$$

$$J_{A_1} = A_3'A_0$$

$$K_{A_1} = A_0$$

$$J_{A_0} = 1$$

$$K_{A_0} = 1$$

D-FF

present

A_3	A_2	A_1	A_0
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

next

A_3	A_2	A_1	A_0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
0	0	0	0

F-F input

D_3	D_2	D_1	D_0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
0	0	0	0

$A_3 A_2$	$A_1 A_0$	00	01	11	10
00	00	0	0	0	0
01	00	0	0	0	0
11	00	x	x	x	x
10	00	1	0	x	x

D_{A_3}

$$D_{A_3} = A_2 A_1 A_0 + A_2 A_1' A_0'$$

$A_3 A_2$	$A_1 A_0$	00	01	11	10
00	00	0	0	0	0
01	00	0	0	0	0
11	00	x	x	x	x
10	00	0	0	x	x

D_{A_2}

$$D_{A_2} = A_2 A_1' + A_2 A_0' + A_2 A_1 A_0$$

$A_3 A_2$	$A_1 A_0$	00	01	11	10
00	00	0	0	0	0
01	00	0	0	0	0
11	00	x	x	x	x
10	00	0	0	x	x

D_{A_1}

$$D_{A_1} = A_3' A_1' A_0 + A_1 A_0'$$

$A_3 A_2$	$A_1 A_0$	00	01	11	10
00	00	0	0	0	0
01	00	0	0	0	0
11	00	x	x	x	x
10	00	1	0	x	x

$D_{A_0} = A_0'$

because J-k F-F use less gates, so it takes up less space, has a clearer logic and is easier to maintain

